

# Basic Electronics (ECE113)

## Tutorial 5

Q1. For each circuit shown in Fig. 1, calculate the voltage labeled  $v_C$ .

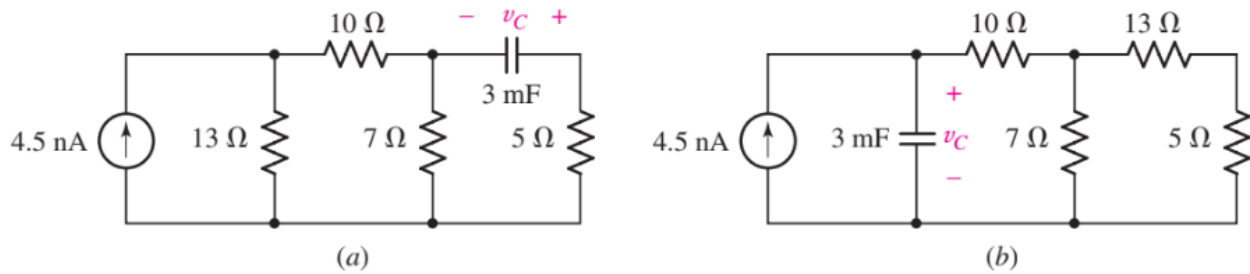


Fig.1

Q2. Calculate  $v_L$  and  $i_L$  for each of the circuits depicted in Fig. 2, if  $i_s = 1 \text{ mA}$  and  $v_s = 2.1 \text{ V}$ .



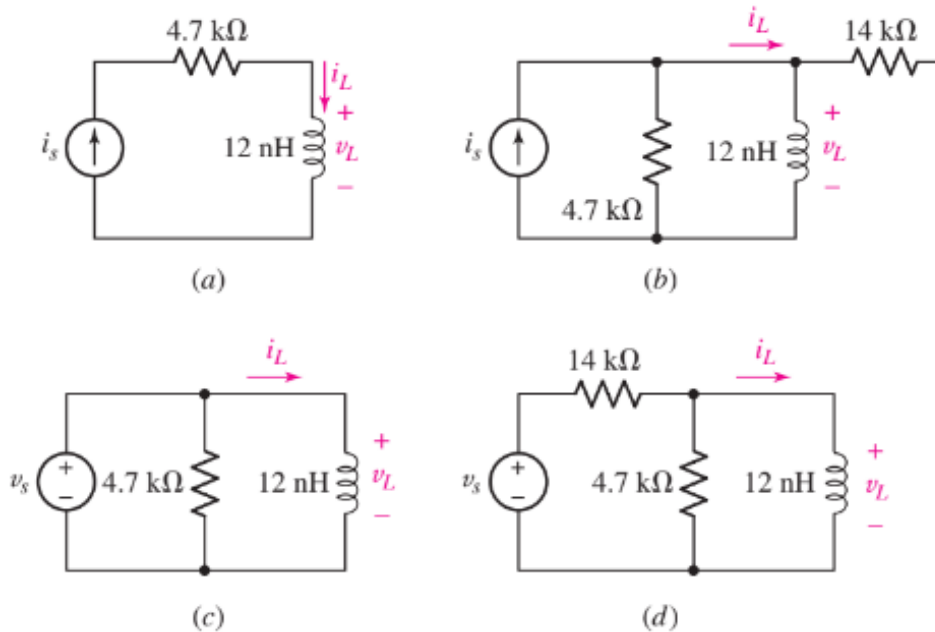


Fig.2

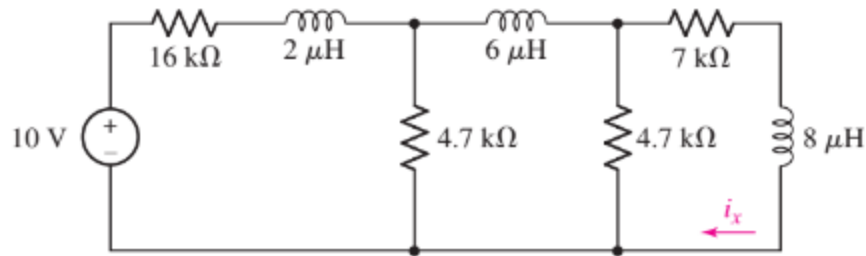Q3. Making the assumption that the circuits in Fig. 3 have been connected for a very long time, determine the value for each current labeled  $i_x$ .



(a)

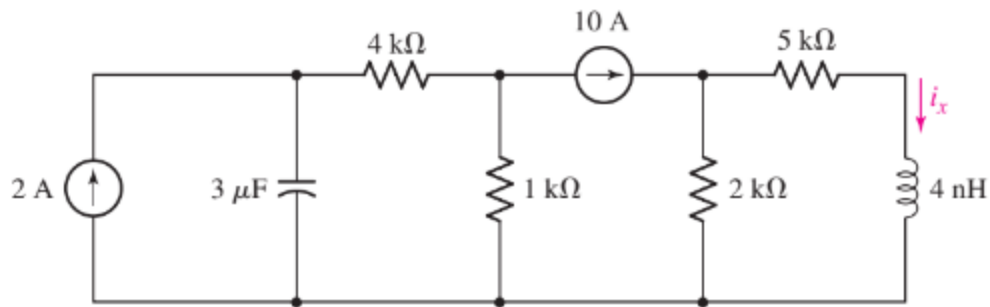

(b)

Fig.3

- Q4. For the circuit shown in Fig. 4,  
 (a) compute the Thévenin equivalent seen by the inductor  
 (b) determine the power being dissipated by both resistors  
 (c) calculate the energy stored in the inductor.

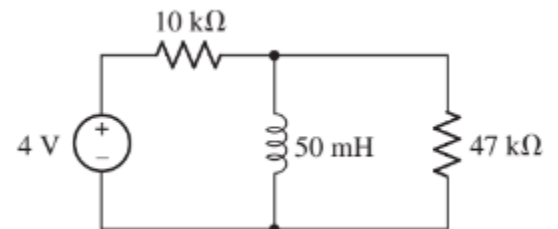


Fig.4

- Q5. Reduce the circuit represented in Fig. 5 to the smallest possible number of components.

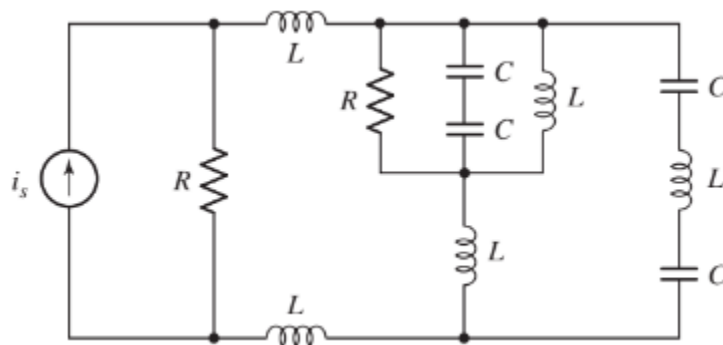


Fig.5

Q6. The switch shown in Fig. 6 has been closed for 6 years prior to being flipped open at  $t=0$ . Determine  $i_L$ ,  $v_L$ , and  $v_R$  at  $t$  equal to (a)  $0^-$  (b)  $0^+$  (c)  $1\ \mu\text{s}$  (d)  $10\ \mu\text{s}$ .

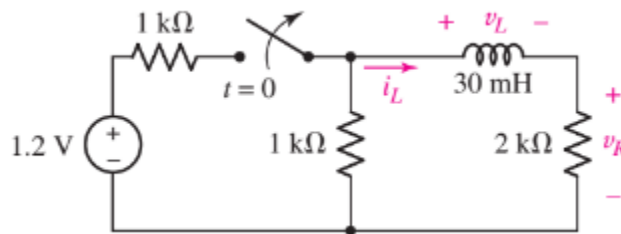


Fig.6

Q7. The circuit depicted in Fig. 7 contains two independent sources, one of which is only active for  $t > 0$ . (a) Obtain an expression for  $i_L(t)$  valid for all  $t$ ; (b) calculate  $i_L(t)$  at  $t = 10\ \mu\text{s}$ ,  $20\ \mu\text{s}$ , and  $50\ \mu\text{s}$ .

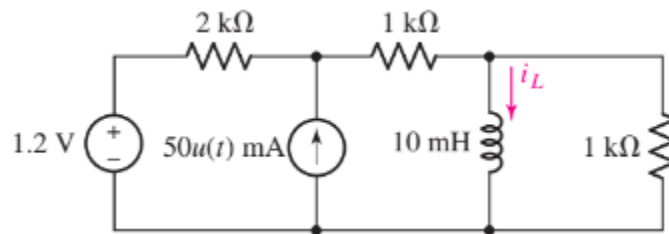


Fig.7

Q8. For the circuit represented in Fig. 8, (a) obtain an expression for  $v$  which is valid for all values of  $t$ ; (b) sketch your result for  $0 \leq t \leq 3\ \text{s}$ .

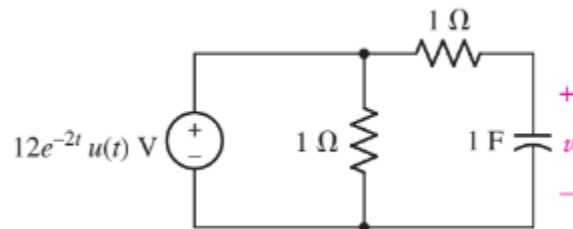


Fig.8