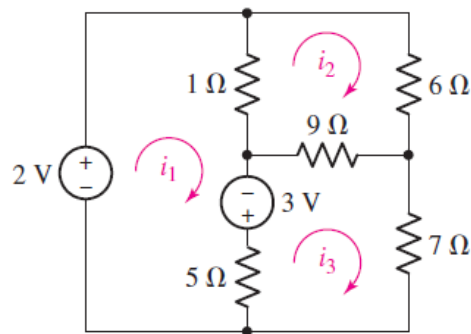


**Basic Electronics ( ECE113 )**  
**Assignment 1**


(40 marks)

- 1) Determine numerical values for each of the three mesh currents as labeled in the circuit diagram shown below:-




(4 marks)

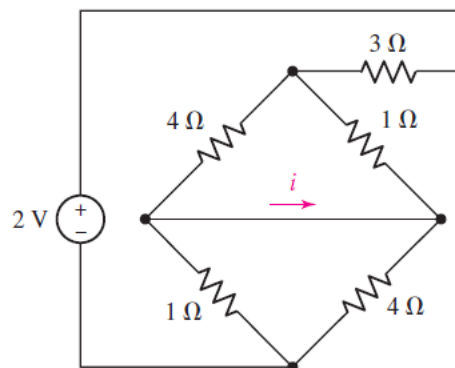- 2) Employing mesh analysis procedures, obtain a value for the current labeled 'i' in the circuit shown below:-



(4 marks)

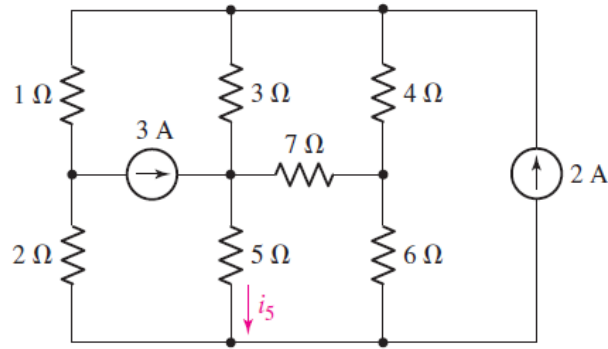
- 3) For the circuit represented below:
- How many nodal equations would be required to determine  $i_5$ ?
  - Alternatively, how many mesh equations would be required?
  - Would your preferred analysis method change if only the voltage across the  $7\Omega$  resistor were needed? Explain.



(6 marks- 2 marks each)

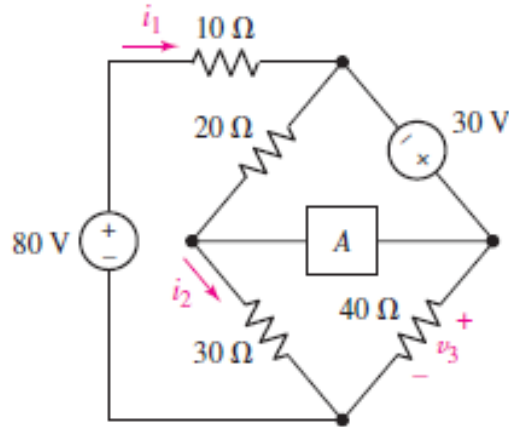
4) Referring to Fig. shown below,

- Determine whether nodal or mesh analysis is more appropriate in determining  $i_2$  if element A is replaced with a short circuit, then carry out the analysis.
- Verify your answer with an appropriate Itspice simulation. Submit a properly labeled schematic along with the answer highlighted.




(6 marks-2 marks each)

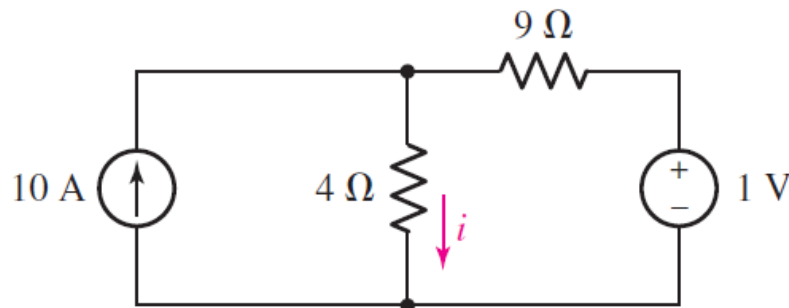- Employ superposition to determine the current labeled 'i' in the circuit shown below.
  - Express the contribution the 1 V source makes to the total current 'i' in terms of a percentage.
  - Changing only the value of the 10 A source, adjust the circuit shown below so that the two sources contribute equally to the current 'i'.




(6 marks- 2 marks each)

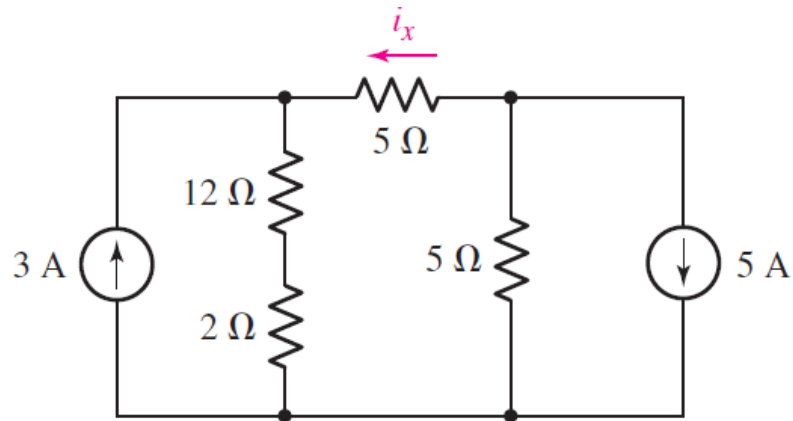- 6) a) Employ superposition to obtain the individual contributions each of the two sources in Fig. shown below makes to the current labeled  $i_x$ .
- (b) Adjusting only the value of the rightmost current source, alter the circuit so that the two sources contribute equally to  $i_x$ .



**(6 marks- 3marks each)**

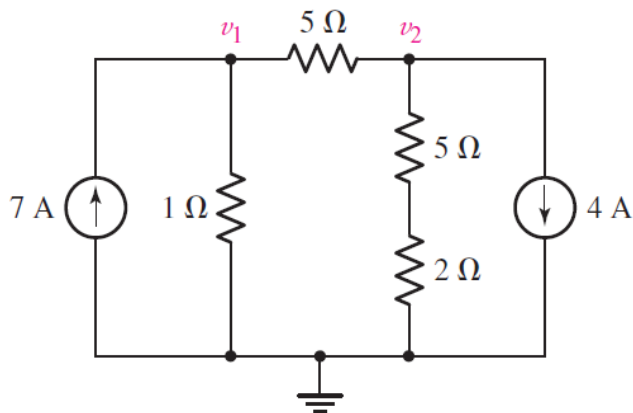- 7) (a) Determine the individual contributions of each of the two current sources in the circuit shown below to the nodal voltage  $v_1$ .
- (b) Determine the percentage contribution of each of the two sources to the power dissipated by the  $2\Omega$  resistor.



**(8 marks- 4 marks each)**