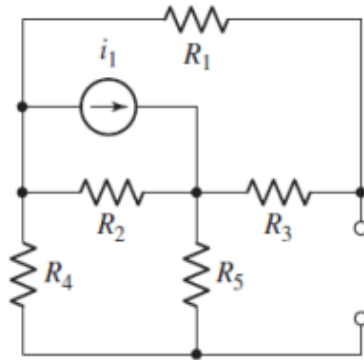


- 1) (a) Employ Thevenin's theorem to obtain a two-component equivalent for the network shown in Fig. shown below.
 (b) Determine the power supplied to a $1\text{ M}\Omega$ resistor connected to the network if $i_1 = 19\text{ }\mu\text{A}$, $R_1 = R_2 = 1.6\text{ M}\Omega$, $R_3 = 3\text{ M}\Omega$, and $R_4 = R_5 = 1.2\text{ M}\Omega$.



31. Select the top of the R_4 resistor as the reference node. v_1 is at the top of R_5 , v_2 is at the “+” of v_{oc} and v_3 is at the “-” of v_{oc} . The bottom node is the negative reference of v_{oc} .

$$\text{Then } i_1 = \frac{v_1}{R_2} + \frac{v_1 - v_3}{R_5} + \frac{v_1 - v_2}{R_3} \quad [1]$$

$$0 = \frac{v_2 - v_1}{R_3} + \frac{v_2}{R_4} \quad [2]$$

$$0 = \frac{v_3 - v_1}{R_5} + \frac{v_3}{R_4} \quad [3] \quad \text{Solving,}$$

$$v_{th} = v_{oc} = v_2 - v_3 = \frac{R_2(R_1R_5 - R_3R_4)i_1}{R_1R_2 + R_1R_4 + R_2R_3 + R_1R_5 + R_2R_4 + R_2R_5 + R_3R_4 + R_3R_5}$$

Next, short the open terminals and define four clockwise mesh currents i_1 , i_2 , i_3 , and i_4 . i_1 is the top mesh, i_3 is the bottom left mesh, i_4 is the bottom right mesh, and i_2 is the remaining mesh. Then

$$-R_2i_2 + (R_2 + R_4 + R_5)i_3 - R_5i_4 = 0 \quad [1]$$

$$-R_3i_1 - R_5i_3 + (R_3 + R_5)i_4 = 0 \quad [2]$$

$$-R_2i_3 + R_2i_2 + R_4i_1 + R_3i_1 - R_3i_4 = 0 \quad [3] \quad \text{and } i_2 - i_1 = i_x \quad [4]$$

Solving, $i_{sc} = i_4 =$


$$\frac{R_2(R_1R_5 - R_3R_4)}{R_1R_2R_3 + R_1R_2R_5 + R_1R_3R_4 + R_1R_3R_5 + R_2R_3R_4 + R_1R_4R_5 + R_2R_4R_5 + R_3R_4R_5} i_1$$

Then, the ratio of v_{th} and i_{sc} yields R_{th} :

$$\frac{R_1R_2R_3 + R_1R_2R_5 + R_1R_3R_4 + R_1R_3R_5 + R_2R_3R_4 + R_1R_4R_5 + R_2R_4R_5 + R_3R_4R_5}{R_1R_2 + R_1R_4 + R_2R_3 + R_1R_5 + R_2R_4 + R_2R_5 + R_3R_4 + R_3R_5}$$

$$(b) V_{oc} = -2.2964\text{ V}; R_{th} = 1.66\text{ M}\Omega. \text{ Hence } P_{1\text{M}\Omega} = \left[\frac{-2.296}{1.66 \times 10^6 + 10^6} \right]^2 (10^6) = 745\text{ nW}$$

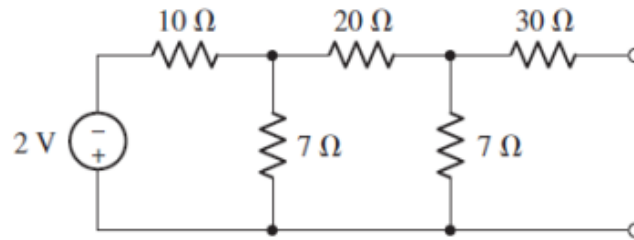- 2) (a) Obtain a value for the Thévenin equivalent resistance seen looking into the open terminals of the circuit shown below by first finding V_{OC} and I_{SC} .
 (b) Connect a 1 A test source to the open terminals of the original circuit after shorting the voltage source, and use this to obtain R_{TH} .
 (c) Connect a 1 V test source to the open terminals of the original circuit after again zeroing the 2 V source, and use this now to obtain R_{TH} .



35. (a) We select the bottom node as the reference node. The top left node is then -2 V by inspection; the next node is named v_1 , the next v_2 , and the far right node is v_{oc} .

$$0 = \frac{v_1 + 2}{10} + \frac{v_1}{7} + \frac{v_1 - v_2}{20} \quad [1]$$

$$0 = \frac{v_2 - v_1}{20} + \frac{v_2}{7} \quad [2]$$

Solving,

$$v_2 = v_{oc} = -185.3 \text{ mV}$$

Next, we short the output terminals and compute the short circuit current. Naming the three clockwise mesh currents i_1 , i_2 and i_{sc} , respectively, beginning at the left,

$$2 + 17i_1 - 7i_2 = 0 \quad [1]$$

$$-7i_1 + 34i_2 - 7i_{sc} = 0 \quad [2]$$

$$-7i_2 + 37i_{sc} = 0 \quad [3]$$

Solving, $i_{sc} = -5.2295 \text{ mA}$.

Hence

$$R_{TH} = \frac{v_{oc}}{i_{sc}} = \boxed{35.43 \Omega}$$

(b) Connecting a 1 A source to the dead network, we can simplify by inspection, but performing nodal analysis anyway:

$$0 = \frac{v_1}{10} + \frac{v_1}{7} + \frac{v_1 - v_2}{20} \quad [1]$$

$$0 = \frac{v_2 - v_1}{20} + \frac{v_2}{7} + \frac{v_2 - v_{test}}{30} \quad [2]$$

$$1 = \frac{v_{test} - v_2}{30} \quad [3]$$

Solving, $v_{test} = 35.43 \text{ V}$ hence $R_{TH} = 35.43/1 = \boxed{35.43 \Omega}$

(c) Connecting a 1 A source, we can write three mesh equations after defining clockwise mesh currents:

$$0 = 17i_1 - 7i_2 \quad [1]$$


$$0 = -7i_1 + 34i_2 - 7i_3 \quad [2]$$

$$-1 = -7i_2 + 37i_3 \quad [3]$$

Solving,

$$i_3 = -28.23 \text{ mA. Thus, } R_{TH} = 1/(-i_3) = \boxed{35.42 \Omega}$$

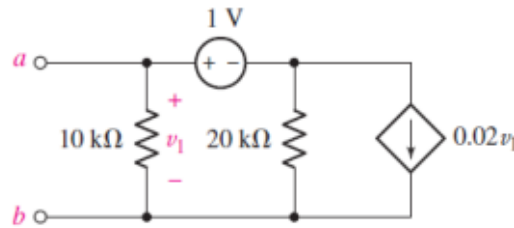- 3.) With regard to the circuit of Fig. 5.82, determine the power dissipated by
 (a) a 1 k Ω resistor connected between a and b ;
 (b) a 4.7 k Ω resistor connected between a and b ;
 (c) a 10.54 k Ω resistor connected between a and b .



41. We define nodal voltage v_1 at the top left node, and nodal voltage v_2 at the top right node. The bottom node is our reference node. By nodal analysis,

$$-0.02v_1 = \frac{v_1}{10 \times 10^3} + \frac{v_2}{20 \times 10^3} \quad [1]$$

$$\text{and } v_2 - v_1 = 1 \quad [2]$$

Solving,

$$v_1 = -2.481 \text{ mV} = v_{oc} = v_{TH}$$

Next, short the 1 V independent source and connect a 1 A source across the open terminals. Define v_{test} across the source with the “+” reference at the arrow head of the source.

Then

$$1 - 0.02v_1 = \frac{v_1}{10 \times 10^3} + \frac{v_1}{20 \times 10^3} \quad [1]$$

$$v_1 = v_{test} = 49.63 \text{ V}$$

Hence,

$$R_{TH} = v_{test}/1 = 49.63 \Omega$$


$$P_{R_L} = \left(\frac{-2.481 \times 10^{-3}}{R_L + 49.63} \right)^2 R_L. \text{ Plugging in resistor values,}$$

(a) 5.587 nW

(b) 1.282 nW

(c) 578.5 pW

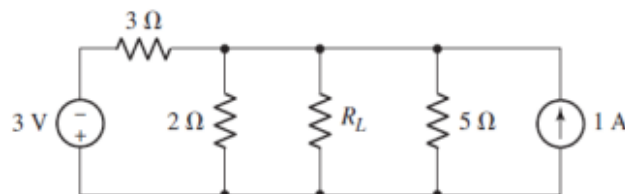- 4) For the circuit of Fig. 5.90, what value of R_L will ensure it absorbs the maximum possible amount of power?



50. We need only R_{TH} . Setting all sources to zero, removing R_L , and looking into the terminals,


$$R_{TH} = 5 \parallel 2 \parallel 3 = 967.7 \text{ m}\Omega$$

Setting $R_L = R_{TH} = 967.7 \text{ m}\Omega$ achieves maximum power delivery.

5.) Referring to the circuit of Fig. 5.92,

(a) determine the power absorbed by the $3.3\ \Omega$ resistor;

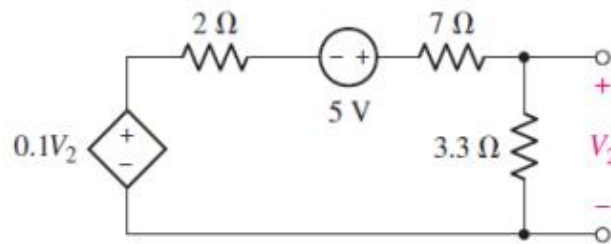(b) replace the $3.3\ \Omega$ resistor with another resistor such that it absorbs maximum power from the rest of the circuit.



(a) Define clockwise mesh current i . Then

$$-0.1v_2 + 2i - 5 + 7i + 3.3i = 0 \quad \text{where} \quad v_2 = 3.3i$$

Hence,

$$-0.1(3.3i) + 12.3i = 5$$

Solving,

$$i = 417.7\text{ mA} \quad \text{and so} \quad v_2 = 1.378\text{ V} = v_{TH}$$

Consequently, $P = (v_2)^2/3.3 = 575.4\text{ mW}$


(b) Find R_{TH} by connecting a 1 A source across the open terminals.

$$1 = \frac{v_2 - 0.1v_2}{9}. \quad \text{Solving, } v_2 = 10\text{ V}.$$

$$\text{Thus, } R_{TH} = v_2/1 = 10\ \Omega$$

Hence, replace the $3.3\ \Omega$ resistor in the original circuit with $10\ \Omega$.

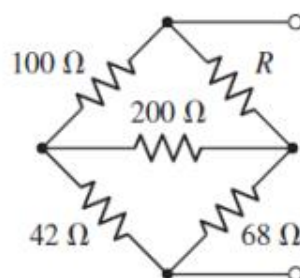6. For the network of Fig. 5.98, select a value of R such that the network has an equivalent resistance of $70.6\ \Omega$.



$$R_A = 42\ \Omega; R_B = 200\ \Omega; R_C = 68\ \Omega.$$

$$\text{Then } R_1 = 27.10\ \Omega, R_2 = 43.87\ \Omega, \text{ and } R_3 = 9.213\ \Omega$$

$$\text{The new network is then } (100 + 27.1) \parallel (R + 43.87) + 9.213 = 70.6\ \Omega$$

Solving, $R = 74.86\ \Omega$