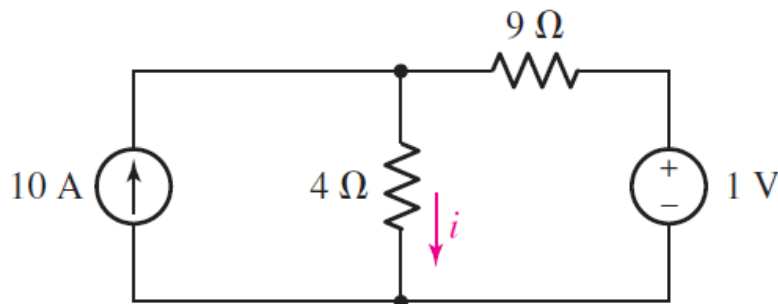


Basic Electronics (ECE113)

Tutorial 3


Q1.

- (a) Employ superposition to determine the current labelled i in the circuit shown below.
- (b) Express the contribution the 1 V source makes to the total current i in terms of a percentage.
- (c) Changing only the value of the 10 A source, adjust the circuit shown below so that the two sources contribute equally to the current i .




Q2.

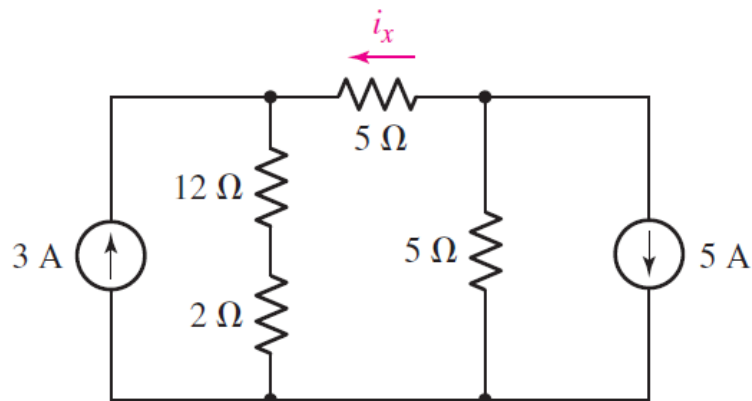- (a) Employ superposition to obtain the individual contributions each of the two sources in Fig. shown below, makes to the current labelled i_x .
- (b) Adjusting only the value of the rightmost current source, alter the circuit so that the two sources contribute equally to i_x .




Q3.

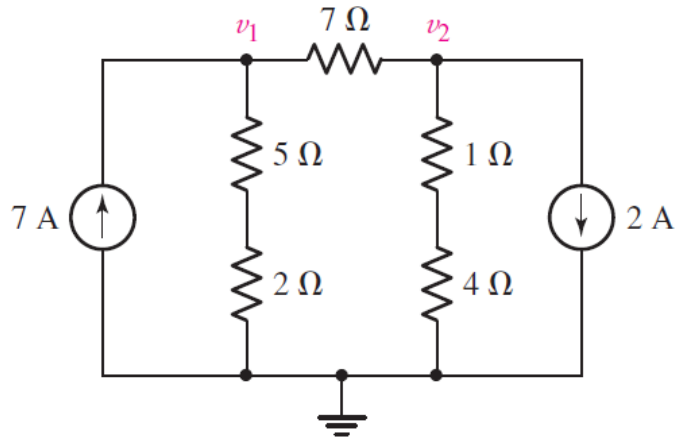- (a) Determine the individual contributions of each of the two current sources shown in Fig. shown below to the nodal voltage labelled v_2 .
- (b) Instead of performing two separate Itspice simulations, verify your answer by using a single dc sweep.




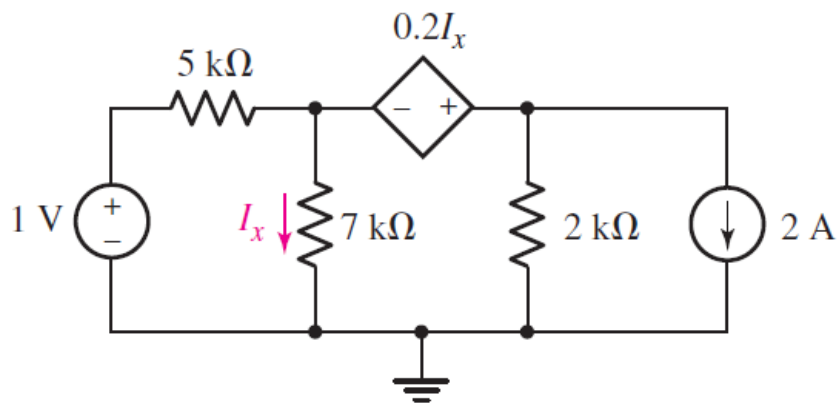Q4. Employ superposition principles to obtain a value for the current I_x as labelled in Fig. shown below



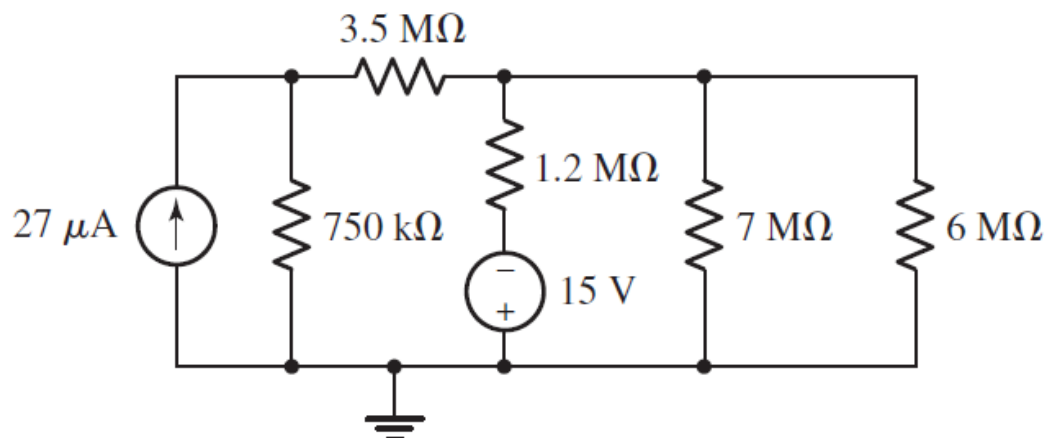Q5.


- Using repeated source transformations, reduce the circuit of Fig. shown below to a voltage source in series with a resistor, both of which are in series with the $6\text{ M}\Omega$ resistor.
- Calculate the power dissipated by the $6\text{ M}\Omega$ resistor using your simplified circuit.



Q6.

(a) Using as many source transformations and element combination techniques as required, simplify the circuit shown below so that it contains only the 7 V source, a single resistor, and one other voltage source.

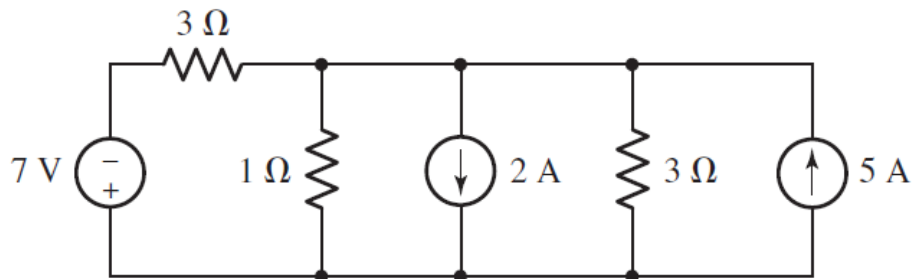(b) Verify that the 7 V source delivers the same amount of power in both circuits.




Q7.

(a) Obtain the Norton equivalent of the network connected to R_L in Fig. shown below

(b) Obtain the Thévenin equivalent of the same network.

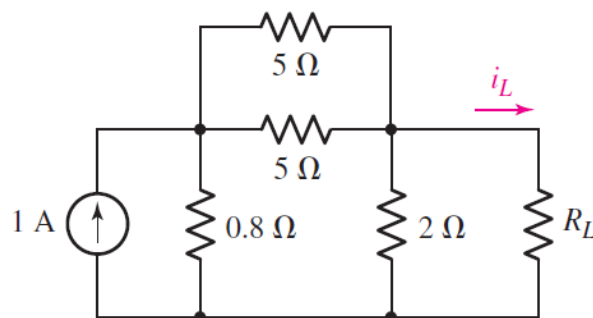(c) Use either to calculate i_L for $R_L = 0\ \Omega$, $1\ \Omega$, $4.923\ \Omega$, and $8.107\ \Omega$.



Q8.

(a) Employ Thevenin's theorem to obtain a simple two-component equivalent of the circuit shown in Fig. shown below.

(b) Use your equivalent circuit to determine the power delivered to a $100\ \Omega$ resistor connected to the open terminals.

(c) Verify your solution by analyzing the original circuit with the same $100\ \Omega$ resistor connected across the open terminals.

