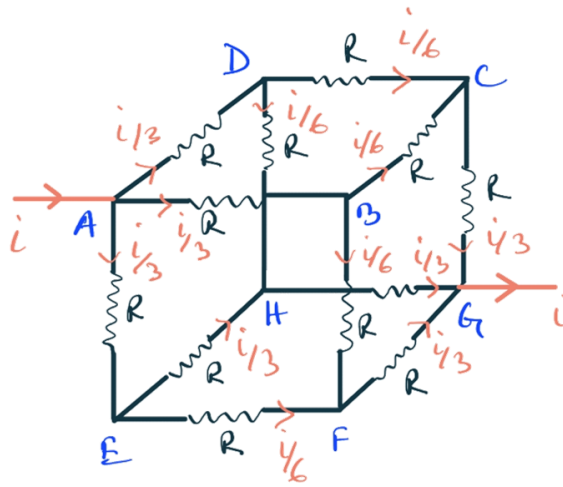


Quiz 1

BE - ECE113

Q1: Solution



Let the current i enter at the point A and leave at the point G. From KCL and by symmetry, the current i at A divides equally along AB, AD and AE. The current in each of these path is therefore $i/3$. Similarly, the current in the three paths HG, FG and CG, which meet at G, are each $i/3$.

Again the currents at B, E, and D divide into two equal parts, each being $i/6$. Thus, all currents in all the twelve resistances forming the cube are determined.

KVL can now be applied to any path between A & G. For example, choosing the path ABCG we have,

$$V = \frac{i}{3} R + \frac{i}{6} R + \frac{i}{3} R = \frac{5}{6} Ri$$

where V is the potential between A & G.


If the effective resistance between A & G is R_{eq} , then

$$V = R_{eq} i \Rightarrow R_{eq} = \frac{5}{6} R$$

Quiz 1

BE - ECE113

Q2: Solution

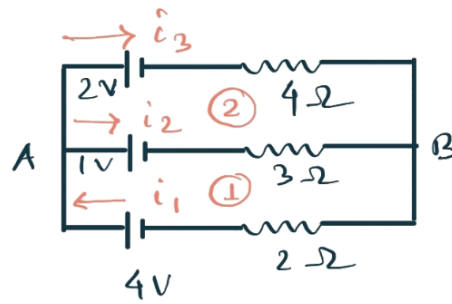

Let i_1, i_2, i_3 be the currents in the three branches as shown in fig.

Applying KCL at point A we obtain,

$$i_1 = i_2 + i_3 \quad \text{--- (I)}$$

We need two more independent eq^s to solve for the three unknowns i_1, i_2, i_3 . These are obtained by applying KVL to loop ① & ②.

For loop ①

$$\rightarrow 4 = 1 + 3i_2 + 2i_1$$

$$\Rightarrow 3i_2 + 2i_1 = 3 \quad \text{--- (II)}$$

For loop ②

$$\rightarrow 1 = 2 + 4i_3 - 3i_2$$

$$\Rightarrow 3i_2 - 4i_3 = 1 \quad \text{--- (IV)}$$

Using ① in ③, we obtain,

$$3i_2 - 4(i_1 - i_2) = 1$$

$$\Rightarrow 7i_2 = 1 + 4i_1 \quad \text{--- (V)}$$

Substituting for i_2 from ④ in eqⁿ ②, we get,

$$2i_1 = -3 \frac{(1 + 4i_1)}{7} + 3$$


$$\Rightarrow \left(2 + \frac{12}{7}\right)i_1 = \frac{-3}{7} + 3$$

$$\Rightarrow i_1 = \frac{9}{13} \text{ A}$$

Quiz 1

BE - ECE113

Q3: Solution

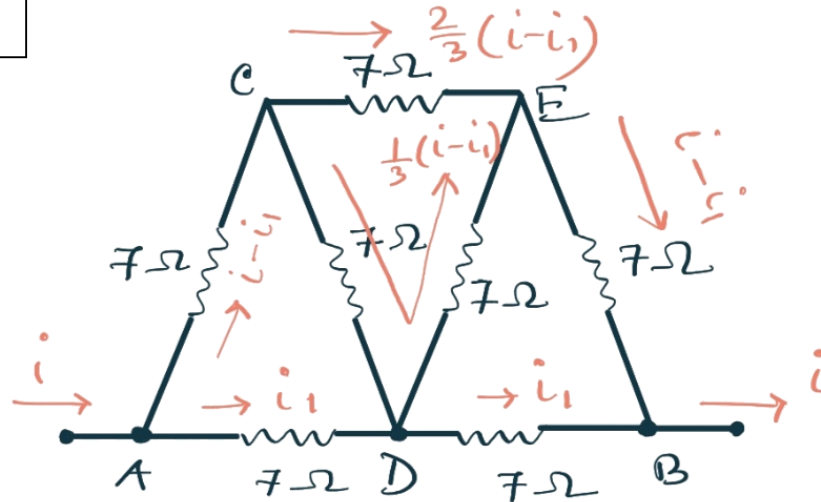

We can redraw the circuit like above.

Here, the arms AD and DB are symmetrically placed; so the arms AC and EB. Hence the current in AC and EB, and those in AD and DB are equal.

Let the current i enter the point A. One part of the current, say i_1 , flows in AD. So, by KCL, the current in AC is $(i - i_1)$. So, the current in DB is i_1 and that in EB is $(i - i_1)$.

The current $(i - i_1)$ in AC is divided at C; a part flows along CE and the rest along CDE. As the resistance of CE is half that of CDE, the current in CE is $\frac{2}{3}(i - i_1)$ and that in CDE is $\frac{1}{3}(i - i_1)$.

Let V is the potential difference between A & B. Consider the path ADB

$$V = 7i_1 + 7i_1 = 14i_1 \quad \text{--- (I)}$$

Considering the path ACB,

$$V = 7(i - i_1) + 7 \times \frac{2}{3}(i - i_1) + 7(i - i_1) \\ = \frac{8}{3} \times 7(i - i_1) \quad \text{--- (II)}$$

Putting the value of i_1 from (I) in (II),

$$V = \frac{56}{3} \left(i - \frac{V}{14} \right) \Rightarrow V = 8i$$

So, the effective resistance between A & B is

$$R_{eq} = \frac{V}{i} = 8 \Omega$$