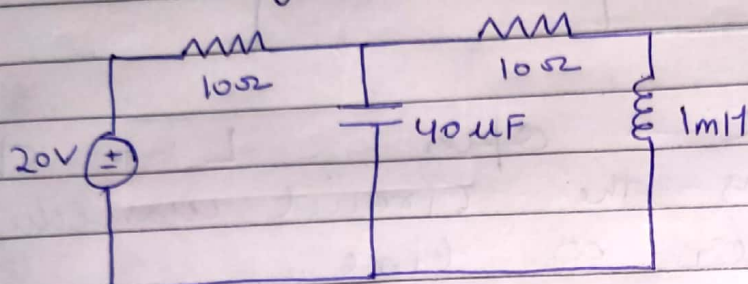


~~for $t < 0$~~

Q-6

~~for $t < 0$~~


for $t < 0$



The circuit has been like this for ∞ .

Inductor \rightarrow short
Capacitor \rightarrow open


~~for $t < 0$~~

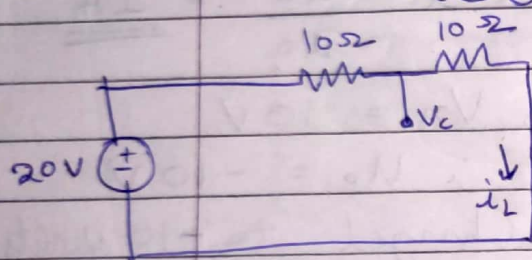

$$i_L(\infty) = 1A \quad V_L(\infty) = 0$$

$$V_C(\infty) = 10 \text{ Volts}$$

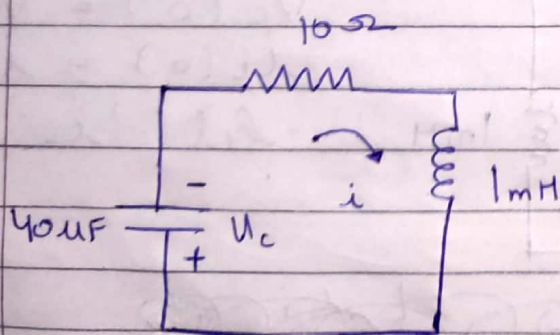The above should be our initial conditions for the natural response of RLC circuit.



We know the 2nd order D.E of Series RLC circuit is given by :-


$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0$$

However for this to happen we need to assume opposite polarity for our capacitor (as shown in figure)

∴ our Initial Condition will change slightly

Although we $\rightarrow V_c(0) = -10$ volts & not $+10$ volts
don't need this

$$i_L(0) = 1A$$

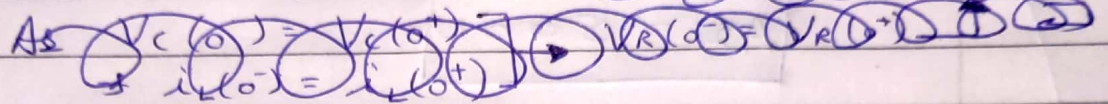

$$i'' + \frac{R}{L} i' + \frac{1}{Lc} i = 0$$

Characteristic Equation :-

$$m^2 + \left(\frac{R}{L}\right)m + \frac{1}{Lc} = 0$$

$$m^2 + 10^4 m + 25 \times 10^6 = 0$$

$$m_1 = m_2 = -5000$$

Critically Damped Case

$$i(x) = A_1 e^{m_1 x} + A_2 x e^{m_2 x}$$

$$i(x) = A_1 e^{-5000x} + A_2 x e^{-5000x}$$

$$i(0) = 1 \text{ Amperes}$$

$$\Rightarrow A_1 e^{-5000(0)} = 1$$

$$\boxed{A_1 = 1}$$

$$i(x) = e^{-5000x} + A_2 x e^{-5000x}$$

$$i'(x) = -5000 e^{-5000x} + A_2 (e^{-5000x} - 5000x e^{-5000x})$$

$$i'(t) = -5000 e^{-5000t} + A_2 e^{-5000t} (1-t)$$

$$V_L = L i'(t)$$

$$\text{at } t=0, \quad V_L = 0$$

$$0 = 10^{-3} (-5000 + A_2)$$

$$A_2 = 5000$$

$$\therefore i_L(t) = e^{-5000t} + 5000t e^{-5000t}$$

$$i_L(t) = e^{-5000t} (1 + 5000t)$$

Amperes

$$\text{at } t=0^+$$

$$V_C = -10 \text{ V}$$

$$i = 1 \text{ A}$$

KVL

$$-V_C - 10i - V_L = 0$$

$$V_L = -(-10) - 10(1)$$

$$V_L = 0 \text{ Volts}$$

Method - 2

(if someone did using V_c)

till m_1, m_2

its Same

Page No. _____

Date _____

$$V_c(t) = A_1 e^{-5000t} + A_2 t e^{-5000t}$$

$$V_c(0) = -10 \text{ Volts}$$

$$\therefore \boxed{A_1 = -10}$$

$$V_c = -10 e^{-5000t} + A_2 t e^{-5000t}$$

$$i_c(0) = 1 \text{ A}$$

$$40 \times 10^{-6} \left(50000 e^{-5000t} + A_2 (e^{-5000t} - 5000t e^{-5000t}) \right)$$

$$40 \times 10^{-6} (5 \times 10^4 + A_2) = 1$$

$$5 \times 10^4 + A_2 = \frac{10^6}{40}$$

$$A_2 = 25 \times 10^3 - 5 \times 10^4$$

$$A_2 = -25000$$

$$V_c = - \left(10 e^{-5000t} + 25000 t e^{-5000t} \right)$$

$$i(t) = C \frac{dV_c}{dt} = 40 \times 10^{-6} e^{-5000t} (5000t + 1)$$

Ampere