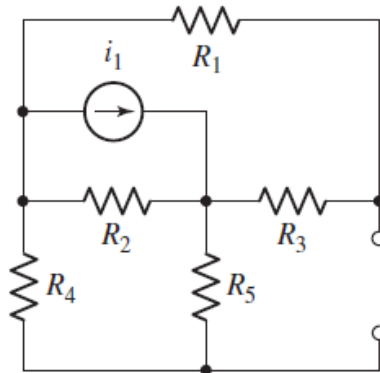



Basic Electronics (ECE113)

Tutorial 4


- 1) (a) Employ Thevenin's theorem to obtain a two-component equivalent for the network shown in Fig. shown below.
 (b) Determine the power supplied to a $1\text{ M}\Omega$ resistor connected to the network if $i_1 = 19\text{ }\mu\text{A}$, $R_1 = R_2 = 1.6\text{ M}\Omega$, $R_3 = 3\text{ M}\Omega$, and $R_4 = R_5 = 1.2\text{ M}\Omega$.



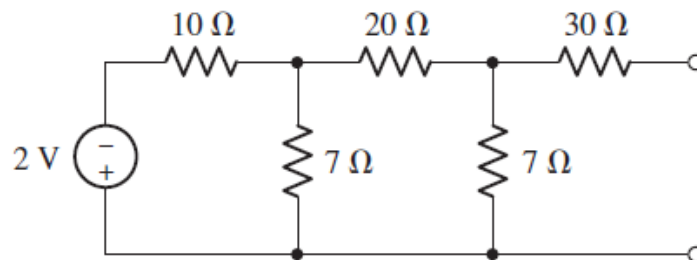- 2) (a) Obtain a value for the Thévenin equivalent resistance seen looking into the open terminals of the circuit shown below by first finding V_{OC} and I_{SC} .
 (b) Connect a 1 A test source to the open terminals of the original circuit after shorting the voltage source, and use this to obtain R_{TH} .
 (c) Connect a 1 V test source to the open terminals of the original circuit after again zeroing the 2 V source, and use this now to obtain R_{TH} .




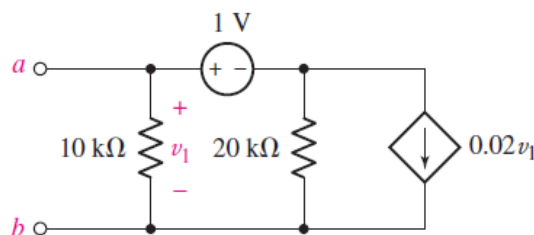- 3.) With regard to the circuit of Fig. 5.82, determine the power dissipated by
 (a) a $1\text{ k}\Omega$ resistor connected between a and b ;
 (b) a $4.7\text{ k}\Omega$ resistor connected between a and b ;
 (c) a $10.54\text{ k}\Omega$ resistor connected between a and b .




■ FIGURE 5.82

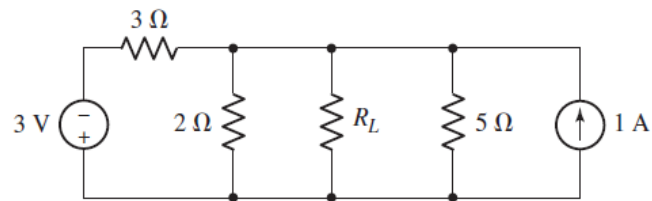- 4) For the circuit of Fig. 5.90, what value of R_L will ensure it absorbs the maximum possible amount of power?




■ FIGURE 5.90

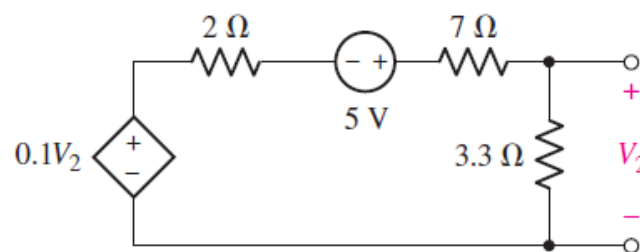- 5.) Referring to the circuit of Fig. 5.92,
 (a) determine the power absorbed by the $3.3\ \Omega$ resistor;
 (b) replace the $3.3\ \Omega$ resistor with another resistor such that it absorbs maximum power from the rest of the circuit.



■ FIGURE 5.92

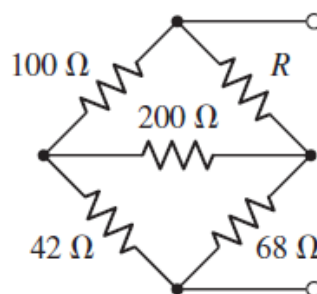6. For the network of Fig. 5.98, select a value of R such that the network has an equivalent resistance of $70.6\ \Omega$.



■ FIGURE 5.98