

Basic Electronics (ECE113) Tutorial 1

1. For the circuit of Fig. 1: -

- (a) Count the number of circuit elements.
- (b) If we move from B to C to D , have we formed a path? Have we formed a loop?
- (c) If we move from E to D to C to B , have we formed a path? Have we formed a loop?

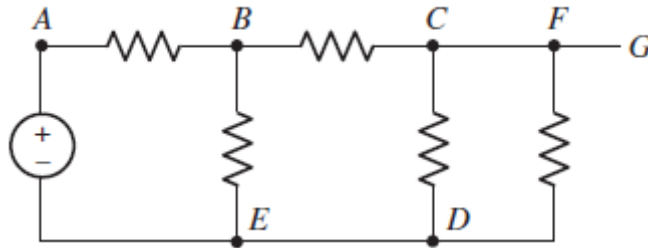


Fig. 1

2. Refer to the circuit of Fig. 2, and answer the following:

- (a) How many distinct nodes are contained in the circuit?
- (b) How many elements are contained in the circuit?
- (c) How many branches does the circuit have?
- (d) Determine if each of the following represents a path, a loop, both, or neither:

- (i) A to B
- (ii) B to D to C to E
- (iii) C to E to D to B to A to C
- (iv) C to D to B to A to C to E



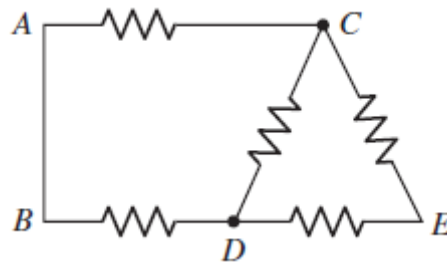


Fig. 2


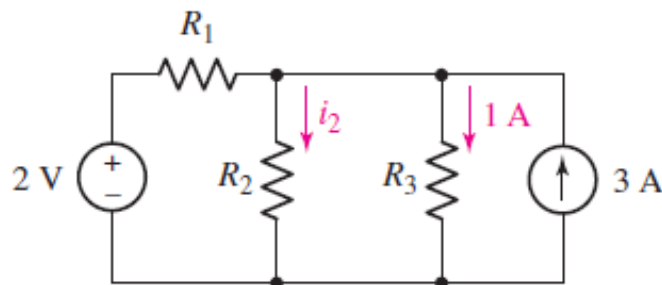
3. In the circuit shown, the resistor values are unknown, but the 2 V source is known to be supplying a current of 7 A to the rest of the circuit. Calculate the current labelled i_2 .



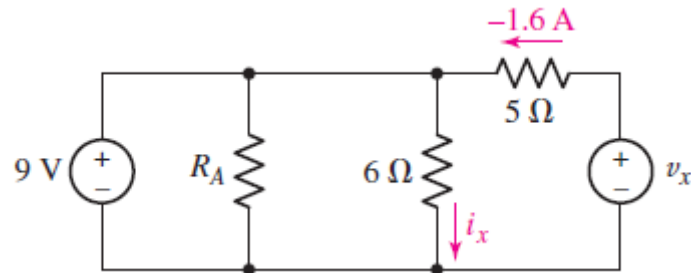
4. In the circuit depicted below, i_x is determined to be 1.5 A, and the 9 V source supplies a current of 7.6 A (that is, a current of 7.6 A leaves the positive reference terminal of the 9 V source). Determine the value of resistor R_A .



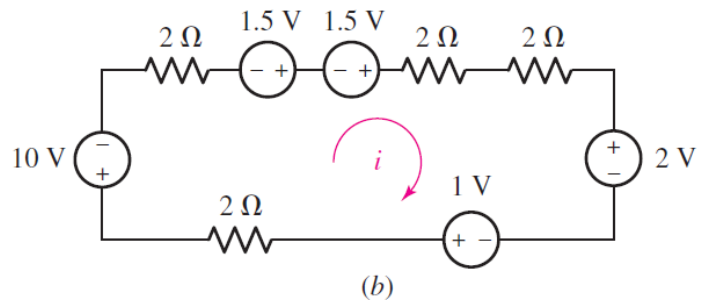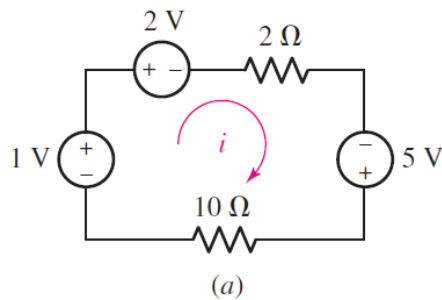
5. Use KVL to obtain a numerical value for the current labelled i in each circuit depicted



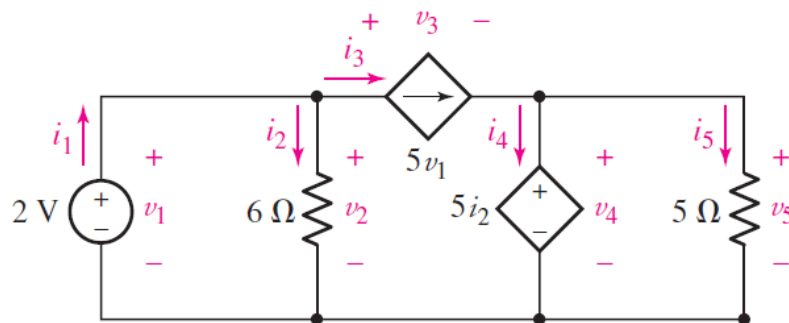
6. (a) Determine a numerical value for each current and voltage (i_1 , v_1 , etc.) in the below circuit.
 (b) Calculate the power absorbed by each element and verify that they sum to zero.



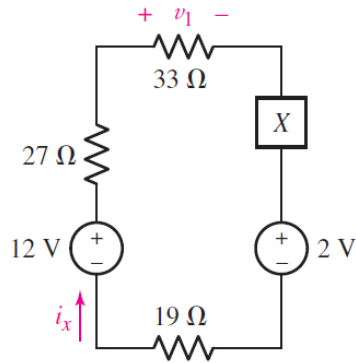
7. Compute the power absorbed by each element in the below circuit if the mysterious element X is
 (a) a $13\ \Omega$ resistor;
 (b) a dependent voltage source labelled $4v_1$, "+" reference on top;
 (c) a dependent voltage source labelled $4i_x$, "+" reference on top.



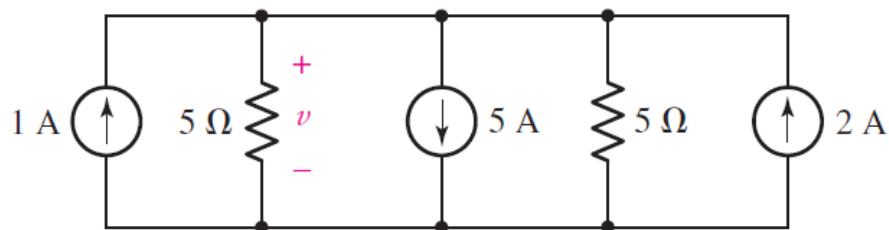
8. Referring to the circuit depicted below, determine the value of the voltage v .



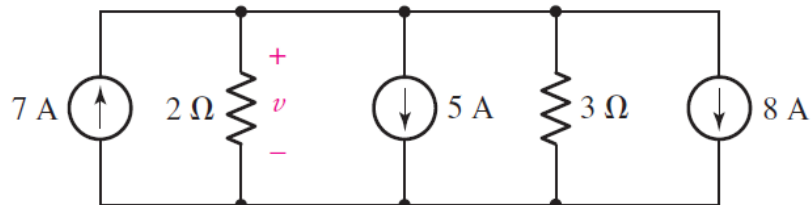
9. (a) For the below circuit, determine the value for the voltage labelled v , after first simplifying the circuit to a single current source in parallel with two resistors.
 (b) Verify that the power supplied by your equivalent source is equal to the sum of the supplied powers of the individual sources in the original circuit.



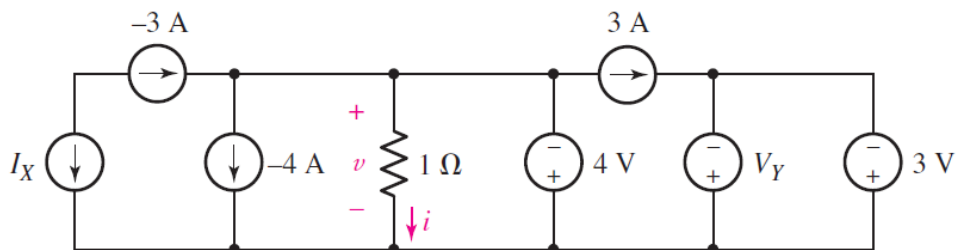
10. (a) Determine the values for I_X and V_Y in the circuit shown below.
 (b) Are those values necessarily unique for that circuit? Explain.
 (c) Simplify the circuit as much as possible and still maintain the values for v and i .
 (Your circuit must contain the $1\ \Omega$ resistor.)



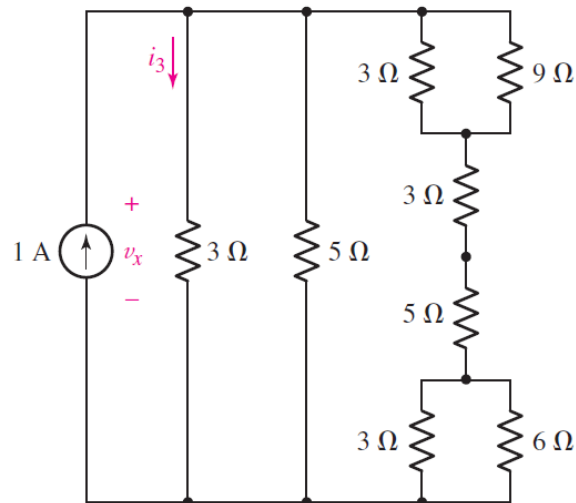11. Making appropriate use of resistor combination techniques, calculate i_3 in the circuit below and the power provided to the circuit by the single current source.



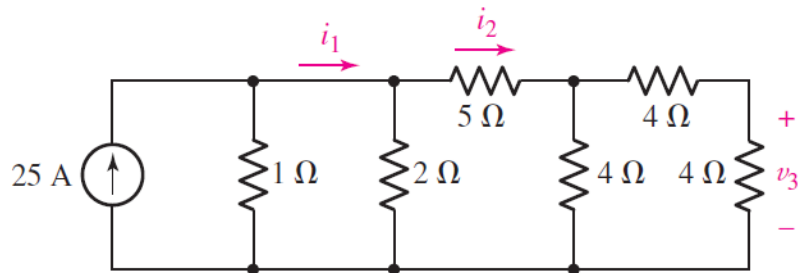12. A network is constructed from a series connection of five resistors having values 1 Ω, 3 Ω, 5 Ω, 7 Ω, and 9 Ω. If 9 V is connected across the terminals of the network, employ voltage division to calculate the voltage across the 3 Ω resistor, and the voltage across the 7 Ω resistor.
13. Employing resistance combination and current division as appropriate, determine values for i_2 , i_3 , and v_3 in the circuit below.



14. The circuit depicted below is routinely employed to model the midfrequency operation of a bipolar junction transistor-based amplifier. Calculate the amplifier output v_{out} if the transconductance g_m is equal to 322 mS.

